

Analysis of RLC Circuits: Serial and Parallel Configurations

IBRAHIM H.I. ABUSHAWISH

Istanbul University, Department of Physics

Instructor: Lect.

Experiment Date: .2024, Report Submission Date: .2024

Course & Section Number: PHYS2305

Abstract—This report presents a comprehensive analysis of RLC circuits, including serial and parallel configurations. It provides a detailed theoretical overview, experimental procedures, data analysis, and discussion of key findings. The analysis is supported by code-based calculations and graphical visualizations produced using Python. Key conclusions indicate that resonance frequency shifts are primarily determined by capacitance in fixed resistance scenarios, while resistance impacts peak sharpness and impedance values. Experimental results revealed resonance peaks at approximately 230 Hz for the parallel RLC circuit with fixed capacitance and 200 Hz for the series RLC circuit with fixed capacitance. Practical implications include the design of frequency filters and oscillators based on RLC circuit configurations.

I. INTRODUCTION

RLC circuits are fundamental in the study of alternating current (AC) electrical systems. They serve as essential components in filters, oscillators, and resonant circuits. This report aims to explore the behavior of both serial and parallel RLC circuits. Key objectives include analyzing the resonance phenomenon, calculating impedance, and visualizing phase shifts. The study emphasizes how resistance, capacitance, and inductance interact under varying frequencies.

II. THEORY

A. Serial RLC Circuit

A serial RLC circuit consists of a resistor (R), inductor (L), and capacitor (C) connected in series. The voltage applied across the circuit can be described as:

$$U(t) = IR + L \frac{dI(t)}{dt} + \frac{Q}{C} \quad (1)$$

where $U(t)$ is the applied voltage, $I(t)$ is the current, R is the resistance, L is the inductance, C is the capacitance, and Q is the charge on the capacitor. Solving for impedance Z , the following expression is obtained:

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \quad (2)$$

The resonance frequency f_0 occurs when the impedance is minimal and is calculated as:

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad (3)$$

At resonance, the current is maximum, and the circuit appears purely resistive.

B. Parallel RLC Circuit

A parallel RLC circuit has R , L , and C elements connected in parallel. The total impedance Z is calculated as:

$$\frac{1}{Z} = \frac{1}{j\omega L} + j\omega C + \frac{1}{R} \quad (4)$$

The condition for resonance in a parallel RLC circuit is when the reactive components cancel each other, leading to:

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (5)$$

The quality factor, bandwidth, and impedance characteristics of parallel RLC circuits are analyzed to identify the conditions for maximum energy transfer.

III. EXPERIMENTAL SETUP

The experimental setup 1 involves several essential components, including resistors, capacitors, and inductors, which are connected to form serial and parallel RLC circuits. An AC power source is used to provide alternating current, and measurements are taken using the Cobra3 PowerGraph software. The circuit diagrams for both serial and parallel RLC circuits are illustrated in Figures 2 and 3, respectively.



Fig. 1: Circuit elements and experimental setup.

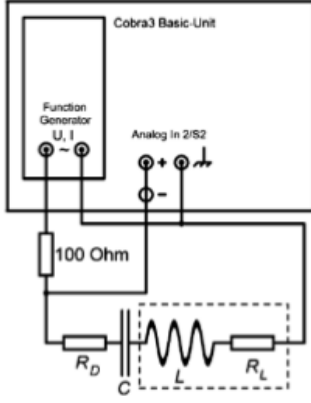


Fig. 2: Circuit diagram of a Serial RLC circuit.

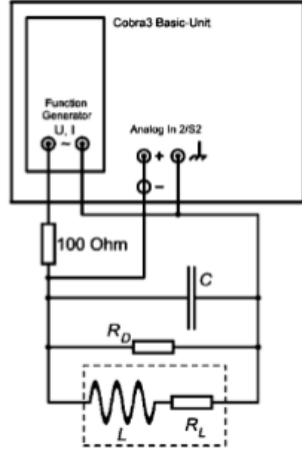


Fig. 3: Circuit diagram of a Parallel RLC circuit.

IV. RESULTS

A. Raw Data

Raw data is available in the GitHub repository [2], in 10th_Experiment_RLC/DATA/.

B. Graphical Analysis

The following figures illustrate the relationship between impedance and frequency for both RLC circuit types, analyzed for fixed capacitance and resistance values. Key resonance peaks are identified and labeled in the graphs.

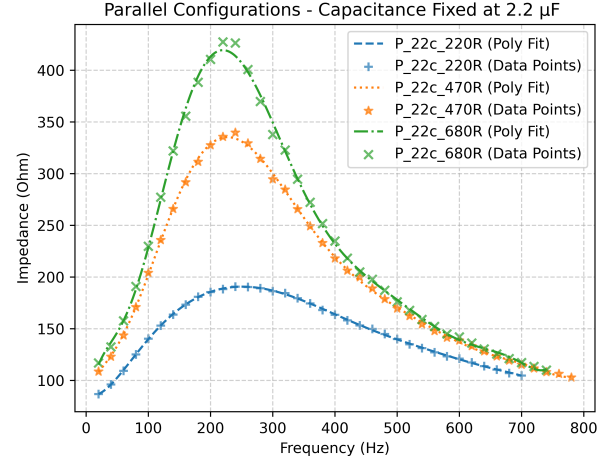


Fig. 4: Parallel RLC circuit with fixed capacitance. The resonance peak is observed at approximately 230 Hz.

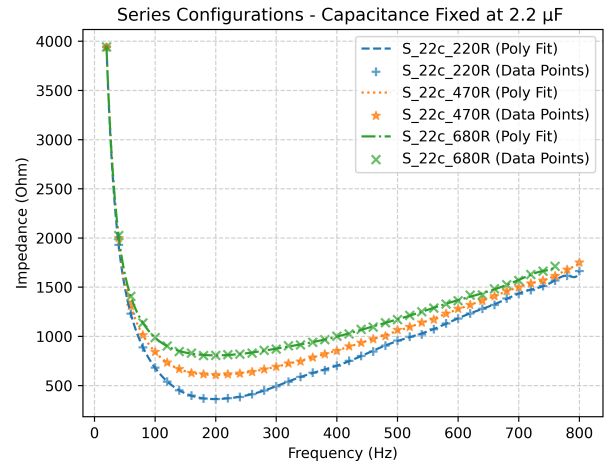


Fig. 5: Serial RLC circuit with fixed capacitance. The resonance peak is observed at approximately 200 Hz.

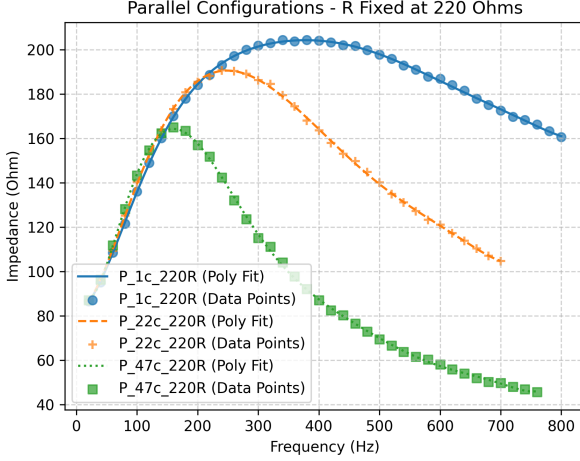


Fig. 6: Parallel RLC circuit with fixed resistance. The resonance peaks are observed at approximately 150 Hz, 250 Hz, and 350 Hz for 4.7 μF , 2.2 μF , and 1 μF capacitance, respectively.

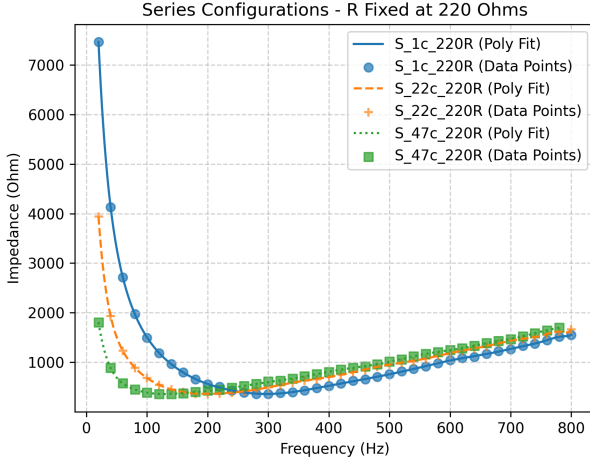


Fig. 7: Serial RLC circuit with fixed resistance. The resonance peaks are observed at approximately 100 Hz, 200 Hz, and 300 Hz for 4.7 μF , 2.2 μF , and 1 μF capacitance, respectively.

V. DISCUSSION

A. Horizontal Shifts

Fixed Resistance, Variable Capacitance: In Figures 6 and 7, resonance frequency shifts horizontally due to the dependence on capacitance: $f_0 = \frac{1}{2\pi\sqrt{LC}}$. Increasing capacitance lowers resonance frequency by increasing the effective reactive impedance.

Fixed Capacitance, Variable Resistance: In Figures 4 and 5, resonance frequency remains constant. However, the sharpness of the resonance peaks is heavily impacted, as resistance directly influences the quality factor Q .

B. Vertical Shifts

Parallel Configurations: Vertical shifts are pronounced in parallel circuits (Figure 4) as impedance at resonance is

inversely proportional to resistance. Higher resistance results in sharper peaks and higher impedance.

Series Configurations: Vertical shifts in series circuits (Figure 5) show increased minimum impedance values with higher resistance, as impedance at resonance aligns with the resistive component of the circuit.

C. Quality Factor Analysis

The quality factor Q determines the sharpness of resonance. Higher Q values are observed for lower resistance in series circuits, reflecting minimal energy dissipation. Conversely, in parallel circuits, the quality factor improves with increased resistance due to enhanced impedance.

D. Practical Implications

These behaviors have significant implications for designing filters and oscillators. For example, in communication systems, parallel RLC circuits with high Q values are used to isolate specific frequency bands, while series circuits are often employed in impedance matching.

VI. CONCLUSION

This experiment provides a comprehensive understanding of RLC circuit behavior, emphasizing the effects of varying resistance and capacitance on resonance. From the discussion, it is evident that resonance frequency shifts are primarily determined by capacitance in fixed resistance scenarios, while resistance impacts peak sharpness and impedance values. Practical insights into designing efficient AC circuit components were highlighted.

VII. ADDITIONAL RESOURCES

For detailed information, including the Lab Manual, source code, and related experiments, visit the GitHub repository provided below or scan the QR code in Fig. 8.



Fig. 8: Access the GitHub repository for the lab manual, source code, and related experiments: <https://github.com/ibeuler/LAB-Reports>.

REFERENCES

- [1] ISTANBUL UNIVERSITY, *Physics Laboratory II Experiment Book: Electricity and Magnetism*, Department of Physics, 2024.
- [2] *Source code and additional experiments are available in the GitHub repository.* <https://github.com/ibeuler/LAB-Reports>