

Determination of Resistance Using Wheatstone Bridge Method

YOUR NAME

ISTANBUL UNIVERSITY FACULTY OF SCIENCE

DEPARTMENT OF PHYSICS

Instructor: INSTRUCTOR NAME

Experiment Date: DD.MM.YYYY , Report Submission Date: DD.MM.YYYY

Course & Section Number: PHYS2305

Abstract—This experiment investigates the resistance measurement of an unknown resistor using the Wheatstone Bridge method and the determination of resistivity based on conductor dimensions. The relationship between resistivity, conductor length, and cross-sectional area is explored. Calculations of resistances, based on various lengths and diameters, verify the theoretical expectations, supporting the use of the Wheatstone Bridge for accurate resistance determination. Results are cross-verified with a hand-drawn graph on millimetric paper.

I. INTRODUCTION

The purpose of this experiment is to measure an unknown resistance using the Wheatstone Bridge and to determine the resistivity based on conductor dimensions. The Wheatstone Bridge is widely used for precise resistance measurements and operates on a balance of voltage in a four-resistor network. Additionally, by measuring resistance and wire dimensions, we can calculate the resistivity, an intrinsic property that affects a material's conductive behavior. Understanding resistivity is essential in material science and circuit design, where it directly impacts current flow and energy efficiency.

II. THEORY

Ohm's Law describes the fundamental relationship between current, voltage, and resistance in a conductor, expressed mathematically as:

$$R = \frac{V}{I} \quad (1)$$

where R is the resistance in ohms, V is the voltage in volts, and I is the current in amperes. This law forms the basis for understanding how resistances behave in an electrical circuit.

In a Wheatstone Bridge configuration, four resistors are arranged in a diamond shape. When the bridge reaches equilibrium—meaning there is no current flowing through the galvanometer connected between the midpoints of two branches—the ratio of the resistances can be expressed as:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad (2)$$

This equation arises from the principle of balance in the bridge, where the potential difference across the galvanometer is zero. The balance condition allows us to determine an unknown resistance R_1 by using known resistances R_2, R_3 , and

R_4 . This relationship is fundamental for accurately measuring unknown resistances in a circuit.

Additionally, the resistivity (ρ) of a conductor, an intrinsic property based on material, relates resistance to its physical dimensions:

$$R = \rho \frac{L}{A} \quad (3)$$

In this equation, R is the resistance, L is the length of the conductor, A is the cross-sectional area, and ρ is the resistivity in ohm-centimeters ($\Omega \cdot \text{cm}$). This formula highlights that resistance increases with length and decreases with a larger cross-sectional area.

In the context of the Wheatstone Bridge, we can also derive another important relationship. Considering the lengths of the segments of the bridge, the ratio of the unknown resistance R_1 to one of the known resistances R_4 can be expressed in terms of the lengths L_2 and L_3 :

$$\frac{R_1}{R_4} = \frac{L_2}{L_3} \quad (4)$$

This derivation stems from the understanding that, at equilibrium, the voltage drop across R_1 is equal to the voltage drop across R_4 . By knowing the lengths L_2 and L_3 , we can effectively calculate the unknown resistance R_1 , further reinforcing the accuracy of the Wheatstone Bridge method in resistance measurement.

The resistivity concept is vital as it affects the conductive properties of materials used in electrical circuits. Understanding the relationship between resistance, resistivity, and physical dimensions of conductors is essential for the design and analysis of electrical systems.

III. EXPERIMENTAL SETUP

The experiment utilizes a Wheatstone Bridge setup to measure an unknown resistance. The equipment includes a galvanometer, voltage source, a known resistance box, and a variable length of resistance wire. Additionally, resistors of different values are used in various configurations to explore the Wheatstone Bridge balance condition. Figure 1 illustrates the Wheatstone Bridge configuration as referenced in the lab manual [1].


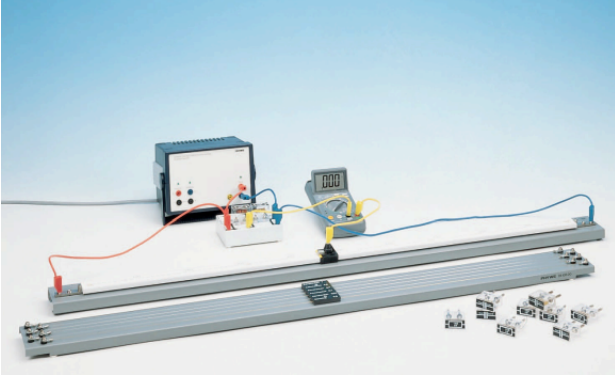



Fig. 1: Wheatstone Bridge Experimental Setup [1].

The first part of the experiment aimed to prove the relationship, $\frac{R_1}{R_4} = \frac{L_2}{L_3}$ as explained in Section IV using the setup shown in Figure 2a.

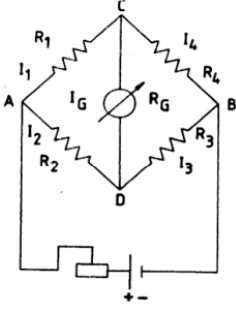while the second part of the experiment aimed to calculate unknown resistances with different configurations with the help of wheatstone bridge as explained in Section IV using the setup shown in Figure 2b.



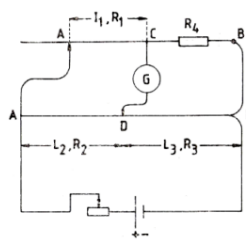(a) Setup with known resistors to verify length-resistance relationships.



(b) Setup with unknown resistors for resistance calculation.

Fig. 2: Wheatstone bridge experimental setups [1].

IV. PROCEDURE

The experiment was conducted in two stages. First, the circuit was set up as shown in Figure 1, with known resistors in a Wheatstone Bridge configuration to verify the relationship in Eq. 4. Various known resistors R_2 were used, and the slider was adjusted along the resistance wire until the galvanometer indicated zero current, signaling a balanced bridge. At this point, the lengths L_2 and L_3 were recorded, and the calculated ratios were compared to verify the relationship between resistance and length.

In the second part, the setup was adjusted to include unknown resistors in place of the known resistors, as shown in Figure 2b. The same process was followed to calculate the unknown resistance R_1 , and as an example, the resistivity was specifically calculated for a wire with a diameter of 0.5 mm, using its length and measured resistance.

V. RESULTS AND DATA

A. Measured Values

Table I presents the recorded lengths and calculated ratios of lengths and resistances for various configurations for known (R_1 , R_4) resistances. The calculations were performed using the formulas derived in the previous sections, as documented in the Calculations.ipynb notebook [2].

R_1 (k Ω)	R_4 (k Ω)	L_2 (cm)	L_3 (cm)	$\frac{R_1}{R_2}$	$\frac{L_2}{L_3}$
4.7	10	31.6	68.4	0.47	0.462
0.330	0.150	68.6	31.4	2.2	2.185

TABLE I: Measured values of resistances and lengths for verifying Eq. 4 in the known-resistor configuration.

The purpose of Table I is that the experimental analysis of eq. 4.

As the second part of the experiment was determination of unknown resistances with different diameters, experimental data was governed and noted on Table II

d (mm)	L_2 (cm)	L_3 (cm)	R_1 (Ω)	R_4 (Ω)
1	61.6	38.4	0.625	1
0.7	43.5	56.5	1.295	1
0.5	28.5	71.5	2.51	1
0.35	15.8	84.2	5.32	1

TABLE II: Measured values of lengths for calculating unknown resistances in the Wheatstone Bridge configuration.

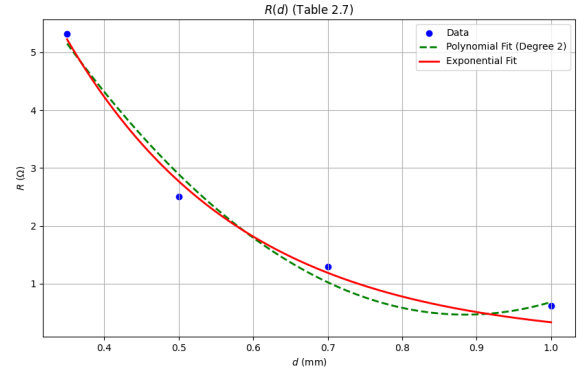


Fig. 3: Plot of Resistance vs. Diameter based on experimental values [1]. The graph is also hand-drawn on millimetric paper, available in the report appendix or repository [3].

B. Resistivity Calculation

As an example, the resistivity (ρ) of a wire with a diameter of 0.5 mm was calculated using its measured resistance and length. Using the measured resistance of $R = 2.770 \Omega$ for a 0.5 mm diameter wire of length $L = 100$ cm, the resistivity was calculated using the following formula:

$$\rho = \frac{R \cdot \pi \cdot \left(\frac{d}{2}\right)^2}{L}$$

Substituting the values, the resistivity ρ was found to be approximately $5.44 \times 10^{-5} \Omega \cdot \text{cm}$. This value is shown in

Table III, consistent with standard resistivity values for the material used.

Diameter (mm)	Length (cm)	ρ ($\Omega\cdot\text{cm}$)
0.5	100	5.44×10^{-5}

TABLE III: Resistivity values for the wire with a diameter of 0.5 mm.

VI. DISCUSSION

The Wheatstone Bridge provided accurate results, closely aligning with theoretical values. Minor discrepancies observed between calculated and expected resistances may result from several sources of error, including contact resistance in the circuit, slight inaccuracies in length measurements, or resistance fluctuations due to temperature changes in the setup. Despite these, the results for resistivity are consistent with standard values, confirming the reliability of the Wheatstone Bridge for precise resistance and resistivity measurements.

VII. CONCLUSION

This experiment successfully applied the Wheatstone Bridge method to determine unknown resistance and measure resistivity. Results support the theory, showcasing the Wheatstone Bridge's precision for such measurements.

VIII. ADDITIONAL RESOURCES

For detailed information, including the Lab Manual, source code, and related experiments, visit the GitHub repository provided below or scan the QR code in Figure ??.

REFERENCES

- [1] ISTANBUL UNIVERSITY, *Physics Laboratory II Experiment Book: Electricity and Magnetism*, Department of Physics, 2024.
- [2] *Source code and additional experiments are available in the GitHub repository.*
Access it at: <https://github.com/ibeuler/LAB-Reports>
- [3] *The graph $R(d)$ fig 3 is also drawn by hand on millimetric paper.*
Available at: and attached to the report.



Fig. 4: Access the GitHub repository for the lab manual, source code, and related experiments: <https://github.com/ibeuler/LAB-Reports>.